

# SERIES RESONANT CIRCUITS

Ashok Ranade, SEAS, Ahmedabad University


# What is a resonant circuit?

- Contains L and C elements
- Either impedance or admittance becomes zero at a frequency called resonant frequency.

# Why resonant circuits?

- Easy to obtain bandpass response with narrow bandwidth
- In narrowband circuits the bandwidth is a small fraction of center frequency
- Examples
  - AM :  $f_c = 1000 \text{ KHz}$  :  $BW = 10 \text{ kHz}$
  - FM :  $f_c = 100 \text{ MHz}$  :  $BW = 200 \text{ kHz}$
  - GSM :  $f_c = 900 \text{ MHz}$  :  $BW = 5 \text{ MHz}$

# Ideal and practical Frequency response

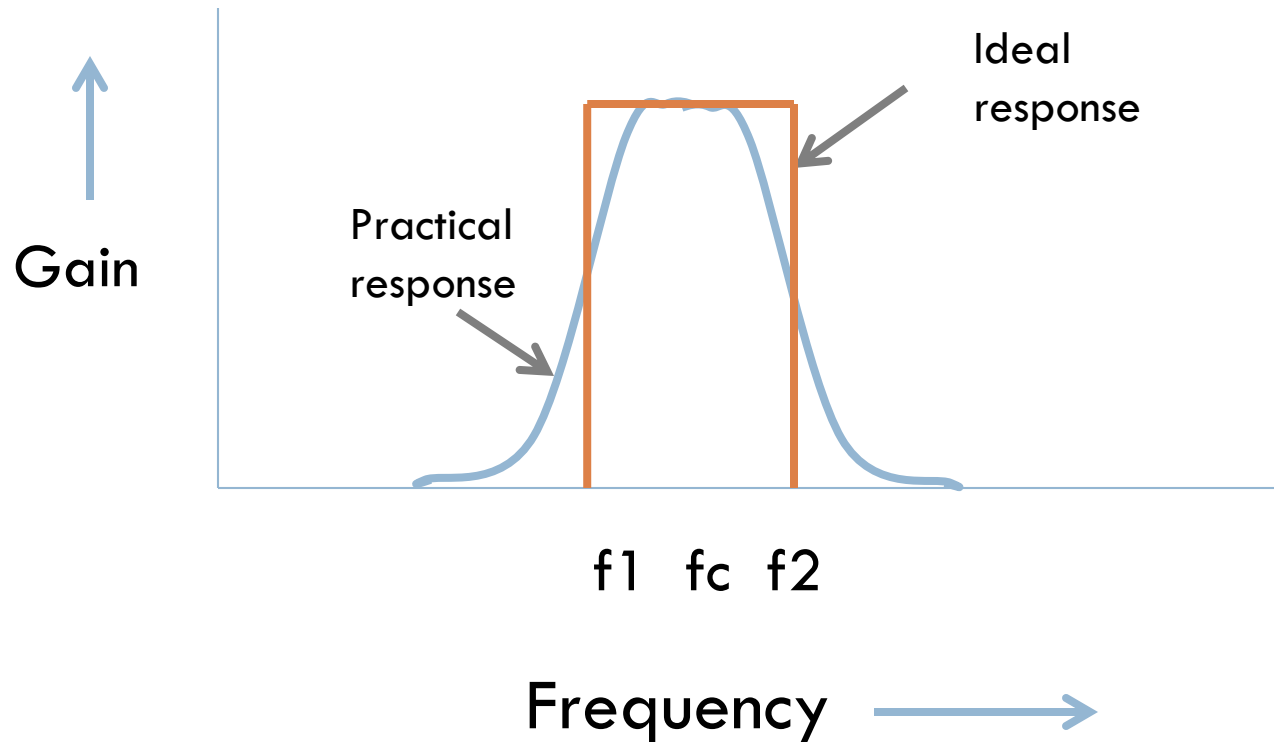

# Series Resonant circuit

- L-C-R are connected in series
- Output is taken across R
- Aims of analysis

Find the resonant frequency

Find the gain at resonant frequency

Find the frequencies at which the gain falls to 0.707

Of the gain at resonance

Hence obtain the expression for bandwidth in terms of  $Q$

# Quality factor

$$\text{Coil } Q = \frac{\omega L}{r}$$


$$\text{Coil } Q = \frac{\omega_0 L}{r}$$

$$\text{Circuit } Q = \frac{\omega_0 L}{r + R}$$

*For ideal coil  $r=0$*

$$\text{Circuit } Q = \frac{\omega_0 L}{R}$$

# Series resonant circuit

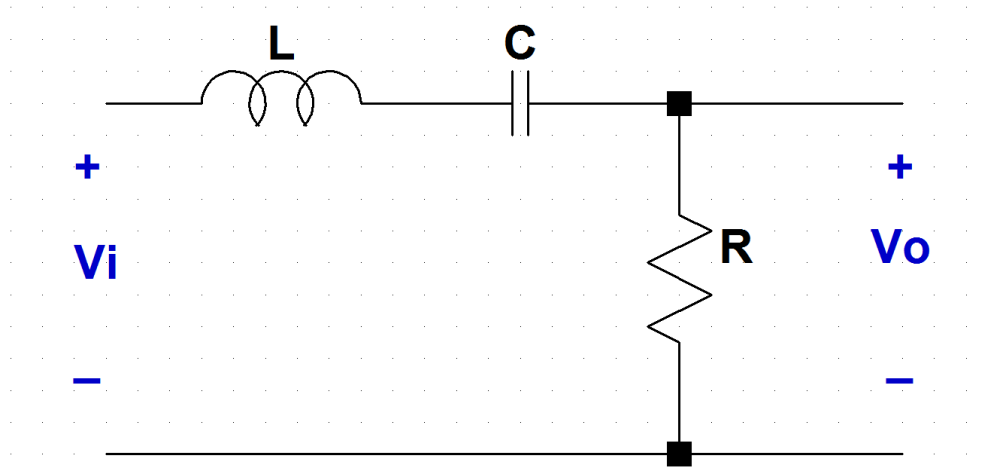

$$V_0 = \frac{V_i R}{R + j\omega L - j / \omega C}$$

$$A = \frac{V_0}{V_i} = \frac{R}{R + j(\omega L - 1 / \omega C)}$$

# Magnitude response

$$|A| = \frac{R}{\sqrt{R^2 + (\omega L - 1/\omega C)^2}}$$


$$\text{At } \omega = \omega_0 : \omega_0 L = 1/\omega_0 C$$

$$|A| = |A|_{\max} = 1$$

$$\omega_0 = \frac{1}{\sqrt{LC}} : f_0 = \frac{1}{2\pi\sqrt{LC}}$$



# Frequency Response

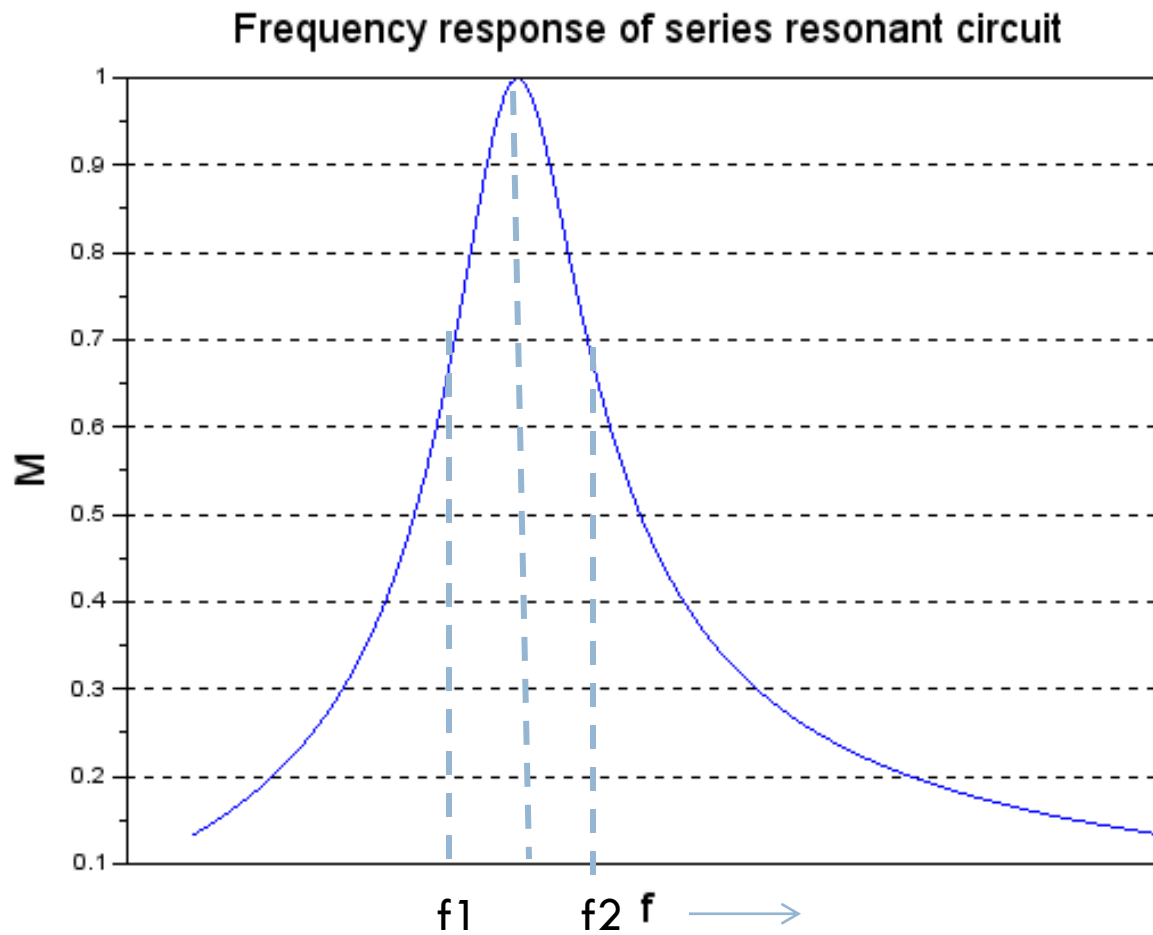

# Bandwidth

$$BW = \omega_2 - \omega_1 \quad A = \frac{1}{1 + j\left(\frac{\omega Q}{\omega_0} - \frac{\omega_0 Q}{\omega}\right)} = \frac{1}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$
$$BW (Hz) = f_2 - f_1$$

$$Q = \frac{\omega_0 L}{R} : \frac{L}{R} = \frac{Q}{\omega_0}$$

$$Q = \frac{1}{\omega_0 CR} : \frac{1}{CR} = \omega_0 Q$$

$$A = \frac{R}{R + j(\omega L - 1/\omega C)} = \frac{1}{1 + j\left(\frac{\omega L}{R} - \frac{1}{\omega CR}\right)}$$

# BW calculation

$$A = \frac{1}{1 + j\left(\frac{\omega Q}{\omega_0} - \frac{\omega_0 Q}{\omega}\right)} = \frac{1}{1 + jQ\left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega}\right)}$$

$$\text{At } \omega = \omega_2 : |A| = \frac{1}{\sqrt{2}}$$

$$\text{Also At } \omega = \omega_1 : |A| = \frac{1}{\sqrt{2}}$$

$$Q\left(\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2}\right) = 1$$

$$Q\left(\frac{\omega_0}{\omega_1} - \frac{\omega_1}{\omega_0}\right) = 1$$

# BW in terms of $\omega_0$ and $Q$

$$\frac{\omega_2}{\omega_0} - \frac{\omega_0}{\omega_2} = \frac{\omega_0}{\omega_1} - \frac{\omega_1}{\omega_0} = \frac{1}{Q}$$

$$\frac{\omega_2^2 - \omega_0^2}{\omega_2 \omega_0} = \frac{1}{Q}$$

$$\frac{\omega_2^2 - \omega_0^2}{\omega_2 \omega_0} = \frac{\omega_0^2 - \omega_1^2}{\omega_1 \omega_0}$$


$$\frac{\omega_2^2 - \omega_1 \omega_2}{\omega_2 \omega_0} = \frac{1}{Q}$$

$$\omega_0^2 = \omega_1 \omega_2$$


$$f_2 - f_1 = \frac{f_0}{Q}$$

$$\omega_2 - \omega_1 = \frac{\omega_0}{Q}$$

# Effect of $Q$ on bandwidth

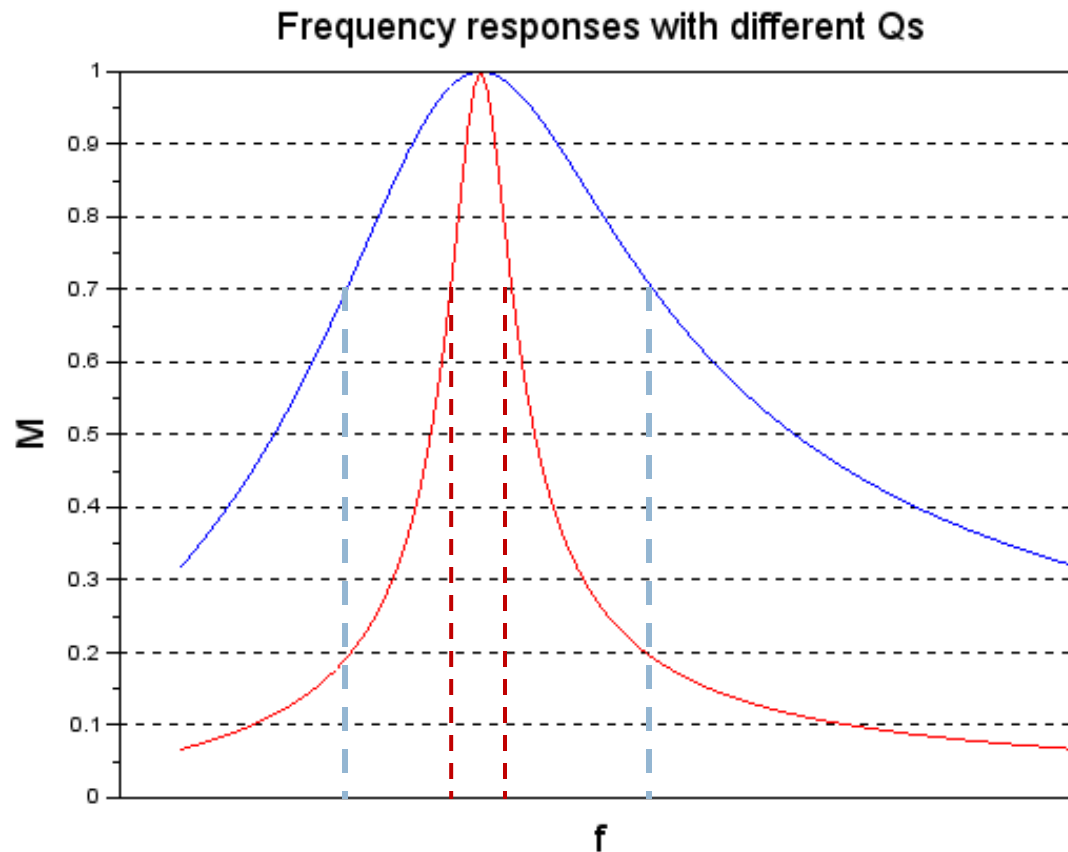

# Effect of series resistance

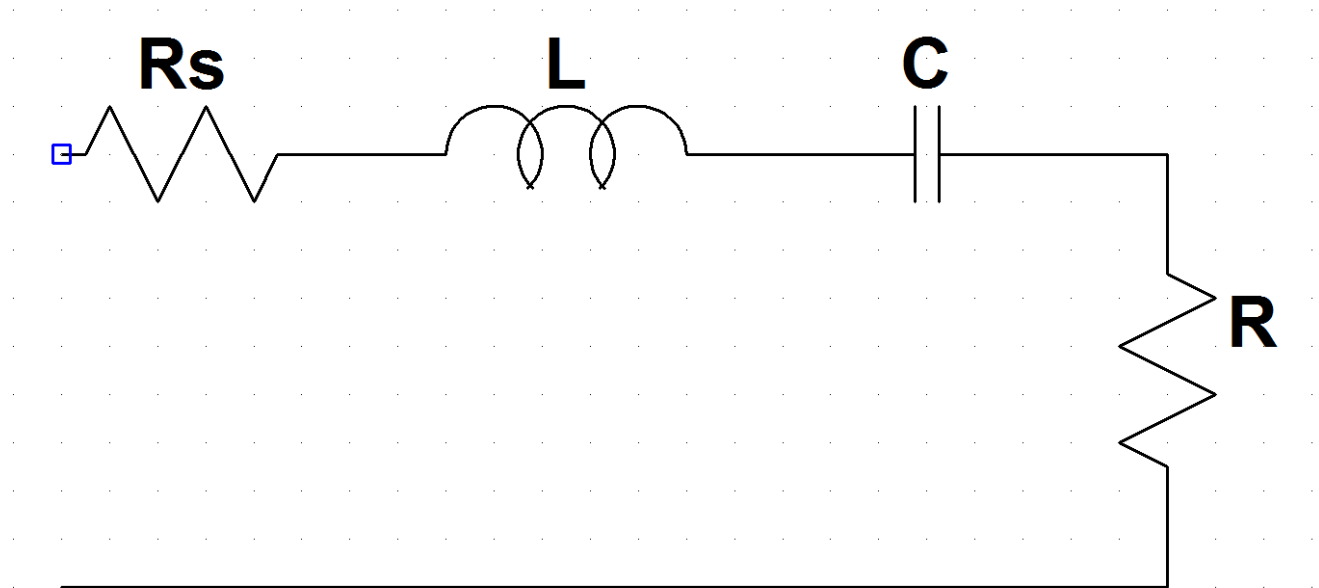

$$A_0 = \frac{R}{R + R_s}$$

$$\text{Effective } Q_{eff} = \frac{\omega_0 L}{R_s + R}$$

# Problem 1

A series RLC circuit has  $f_0 = 5 \text{ MHz}$ ,  $\text{BW} = 100 \text{ kHz}$  and  $R = 50 \text{ ohms}$ . Find out  $L$  and  $C$

$$L = 79.577 \text{ microhenries}$$

$$C = 12.732 \text{ pF}$$

# LTspice

---

- Simulate circuit of problem 1 in LTspice and test its frequency response



# Problem 2

- For a series resonant circuit prove that

$$\frac{|A(n\omega_0)|}{|A(\omega_0)|} \approx \frac{n}{Q(n^2 - 1)}$$

*When  $Q \gg 1$*

# Solution to Problem 2

$$A = \frac{1}{1 + jQ \left( \frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right)}$$

$$|A(n\omega_0)| = \frac{1}{\sqrt{1 + Q^2 \left( n - \frac{1}{n} \right)^2}}$$

$$A(n\omega_0) = \frac{1}{1 + jQ \left( \frac{n\omega_0}{\omega_0} - \frac{\omega_0}{n\omega_0} \right)}$$

When Q is large

$$|A(n\omega_0)| \approx \frac{1}{Q \left( n - \frac{1}{n} \right)} = \frac{n}{Q(n^2 - 1)}$$

$$A(n\omega_0) = \frac{1}{1 + jQ \left( n - \frac{1}{n} \right)}$$

# Solution to Problem 2 continued

$$|A(n\omega_0)| \approx \frac{1}{Q\left(n - \frac{1}{n}\right)} = \frac{n}{Q(n^2 - 1)}$$

Now  $|A(\omega_0)| = 1$

$$\frac{|A(n\omega_0)|}{|A(\omega_0)|} = \frac{n}{Q(n^2 - 1)}$$

# Problem 3

- In a series resonant circuit what must be the minimum  $Q$  for the amplitude of the 5<sup>th</sup> harmonic to be 40 dB below the amplitude of the fundamental frequency

$$Q = 20.83$$

# Solution to Problem 3

$$\frac{|A(jn\omega_0)|}{|A(j\omega_0)|} = \frac{n}{Q(n^2 - 1)} : 20 \log \frac{n}{Q(n^2 - 1)} = -40$$

$$\log \frac{5}{Q(25 - 1)} = -2 : \log \frac{24Q}{5} = 2$$

$$\frac{24Q}{5} = 100 : Q = \frac{500}{24} = 20.83$$