


FREQUENCY CONVERTERS

Lecture 6

Frequency converters

- Frequency converter is used to change the center frequency of a modulated signal
- Modulated signal
$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$
$$y(t) = k_c A(t) \cos[\omega_d t + \theta(t)]$$
- If ω_d is higher than ω_c it is called an up converter
- If ω_d is lower than ω_c it is called a down converter
- Achieved by multiplier followed by filter

Block diagram of a Frequency converter

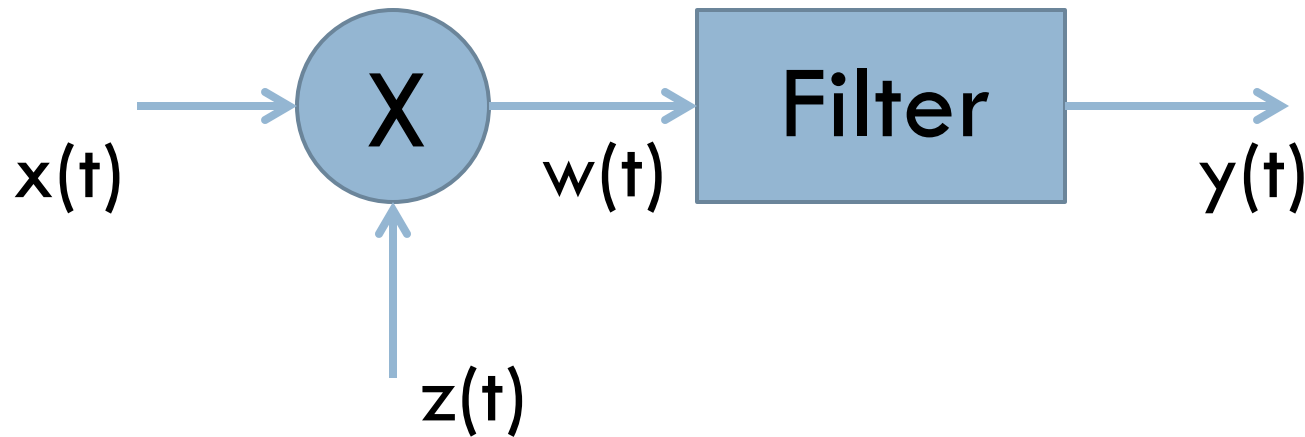


$$w(t) = k_m x(t) z(t)$$

$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$

$$z(t) = A_0 \cos \omega_0 t$$

Block diagram of a converter

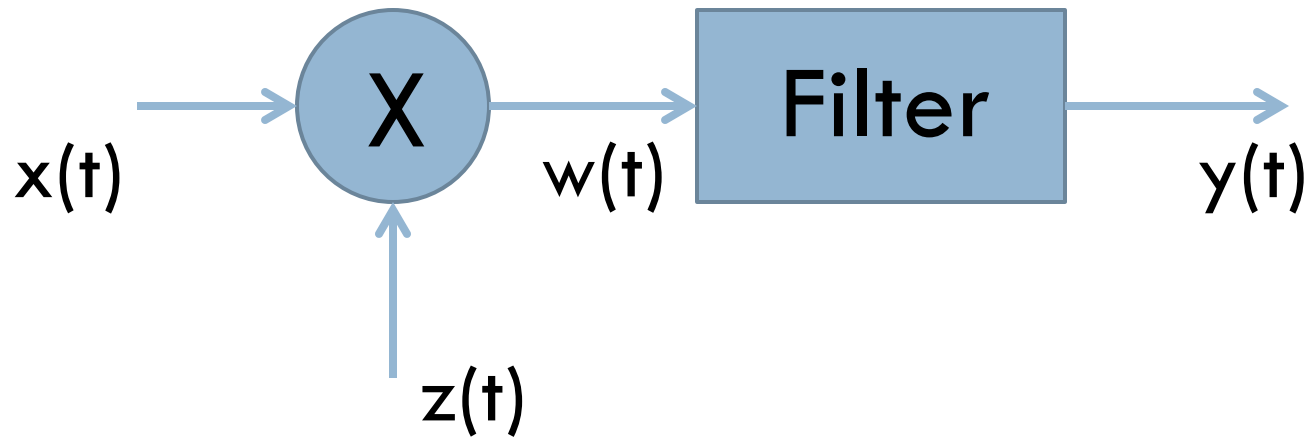

$$w(t) = k_m A(t) \cos[\omega_c t + \theta(t)] \cdot A_0 \cos \omega_0 t$$

$$w(t) = \frac{k_m A(t) A_0}{2} \cos[(\omega_0 + \omega_c)t + \theta(t)] + \frac{k_m A(t) A_0}{2} \cos[(\omega_0 - \omega_c)t - \theta(t)]$$

$$y(t) = \frac{k_m k_f A(t) A_0}{2} \cos[(\omega_0 - \omega_c)t + \theta(t)]$$


Frequency converter

- If the filter selects $\omega_c + \omega_0$ the circuit is an up converter
- If the filter selects $\omega_0 - \omega_c$ then the circuit is called a down converter
- Frequency conversion does not affect the modulation (Waveshape of neither $A(t)$ or $\theta(t)$ is changed)

Frequency multiplier

- This circuit multiplies the carrier frequency of the input by a factor of n
- If input frequency is f_c then output carrier is nf_c
- Achieved by a non-linear device followed by a band-pass filter

Frequency multiplier

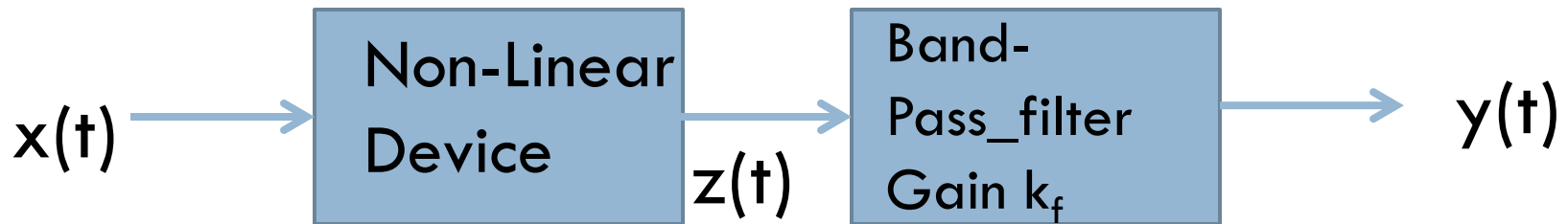

$$z(t) = a x(t) + b x^2(t) + c x^3(t) + \dots$$

$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$

Frequency Doubler

$$z(t) = a x(t) + b x^2(t)$$

$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$

$$z(t) = aA(t) \cos[\omega_c t + \theta(t)] + bA^2(t) \cos^2[\omega_c t + \theta(t)]$$

$$z(t) = aA(t) \cos[\omega_c t + \theta(t)] + \frac{bA^2(t)}{2} \{1 + \cos[2\omega_c t + 2\theta(t)]\}$$

$$y(t) = k_f \frac{b}{2} A^2(t) \{\cos[2\omega_c t + 2\theta(t)]\}$$

Frequency doubler

- Note that the carrier frequency is doubled
- Amplitude is distorted
- Phase is not distorted but doubled
Frequency is also doubled.
- Can be used for changing the carrier of frequency or phase modulated signal but not for amplitude modulated signal

Frequency multiplication by “n”


$$z(t) = a x(t) + b x^2(t) + c x^3(t) + \dots + k x^n(t)$$

$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$

$$z(t) = k_n A^n(t) \cos\{[n\omega_c t + n\theta(t)]\} + \textit{other terms}$$

$$y(t) = k_n k_f A^n(t) \cos\{[n\omega_c t + n\theta(t)]\}$$

Frequency multiplier circuit

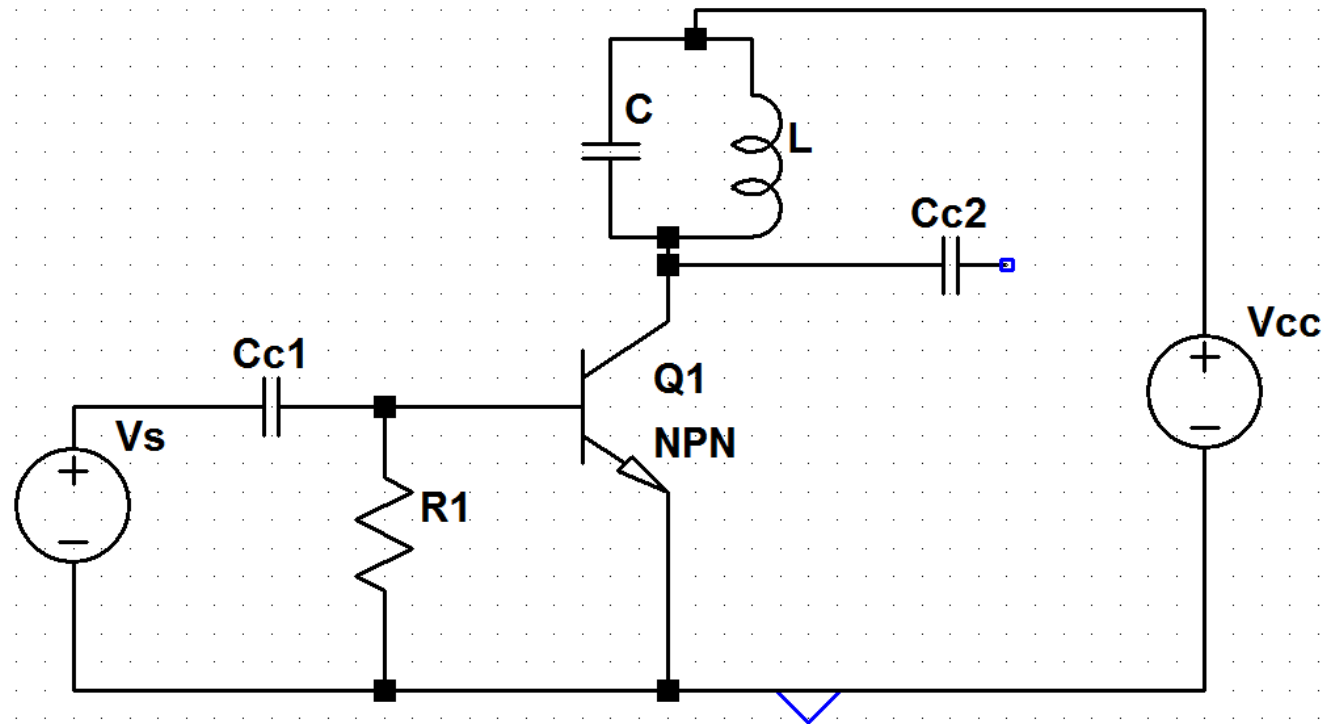


Cascade of frequency multiplier and frequency converter

$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$

The requirement is

$$y(t) = kB(t) \cos[n_1 \omega_c t + n_2 \theta(t)]$$

The block diagram

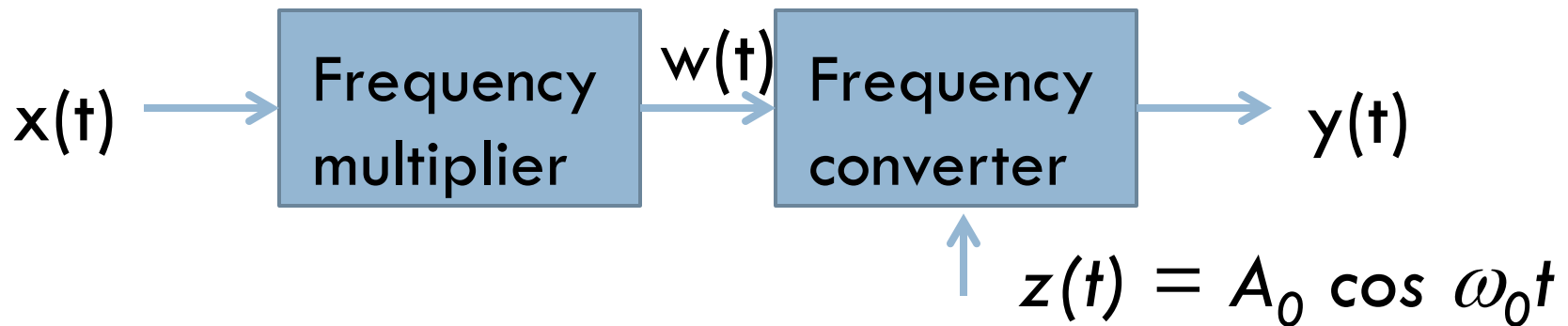


$$x(t) = A(t) \cos[\omega_c t + \theta(t)]$$

$$w(t) = k_m B(t) \cos\{n_2 \omega_c t + n_2 \theta(t)\}$$

$$y(t) = k B(t) \cos\{n_1 \omega_c t + n_2 \theta(t)\}$$

$$\omega_0 - n_2 \omega_c = n_1 \omega_c$$

Problem

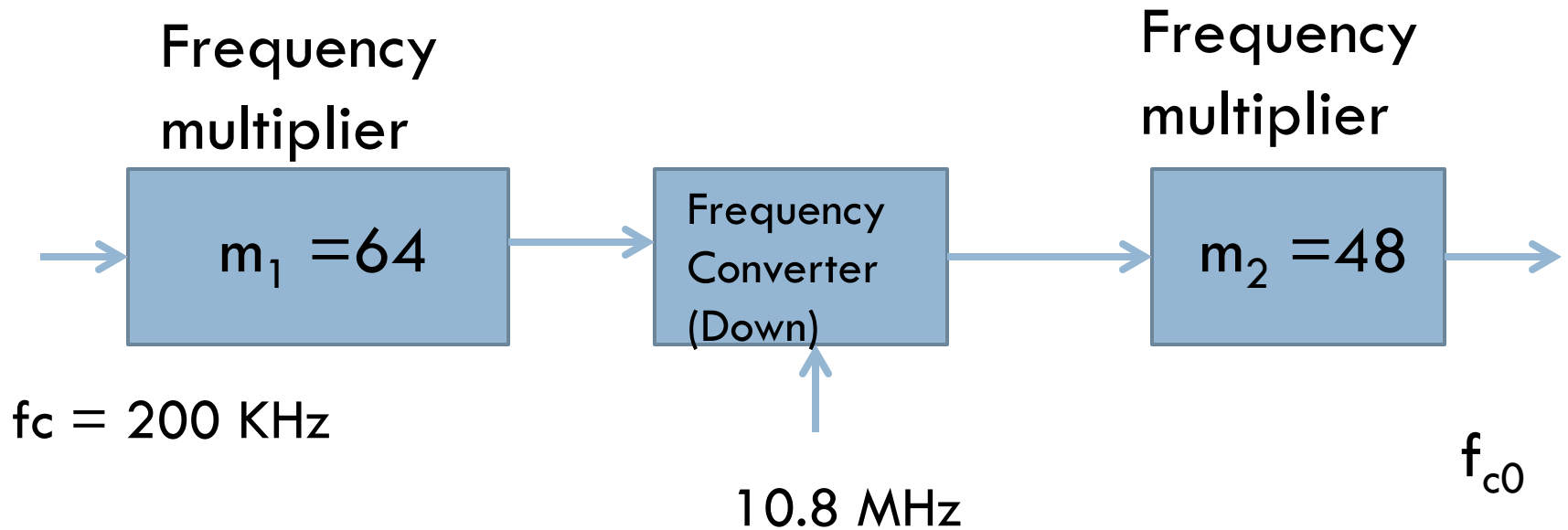

Find out f_{c0} and n_1 and n_2

Solution

The output of the first multiplier has frequency

$$f_{c1} = 0.2 \times 64 = 12.8 \text{ MHz}$$

The frequency at the output of frequency converter

$$12.8 - 10.8 = 2 \text{ MHz}$$

The frequency at the output of second multiplier

$$2 \times 48 = 96 \text{ MHz}$$

$$n_1 = \frac{96}{0.2} = 480$$

$$n_2 = 64 \times 48 = 3072$$

Problem

- 200 Khz to be converted to 96 Mhz
- Only frequency triplers are to be used
- n^2 is not specified

Solution

□ Three blocks in cascade

(1) 4 Frequency triplers

$$n1 = 81$$

The output frequency is $81 \times 0.2 = 16.2 \text{ Mhz}$

(2) UP converter with reference $f_0 = 15.8 \text{ Mhz}$

The output frequency is 32 Mhz

(3) 1 tripler

The output frequency is $32 \times 3 = 96 \text{ Mhz}$

Use of frequency converters in radio transmitters and Receivers

□ Transmitter

200 Khz crystal oscillator


The output frequency required 100 MHz

Frequency converters used

□ Receiver

To understand this we first study RF receiver

Tuned RF receiver

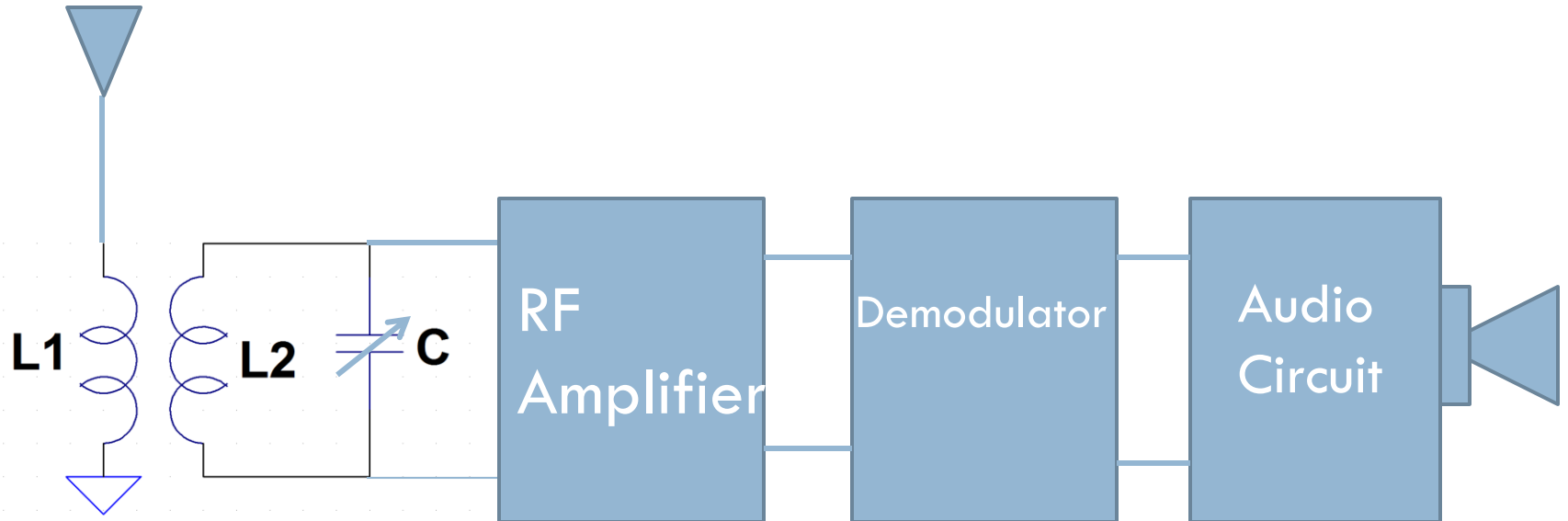

Disadvantages of TRF receivers


- High Q requirement in RF amplifier tank circuit
 $f_c = 100 \text{ MHz} : BW = 200 \text{ Khz}$
 $Q = 100/0.2 = 500$: Rather large
- To get large gain many stages are cascaded so many tank circuits have to be simultaneously tuned.

Multisection gangs were used

- To avoid oscillations neutralization might have to be used

Different neutralizing circuits for different frequencies

Frequency converter in Radio Receiver

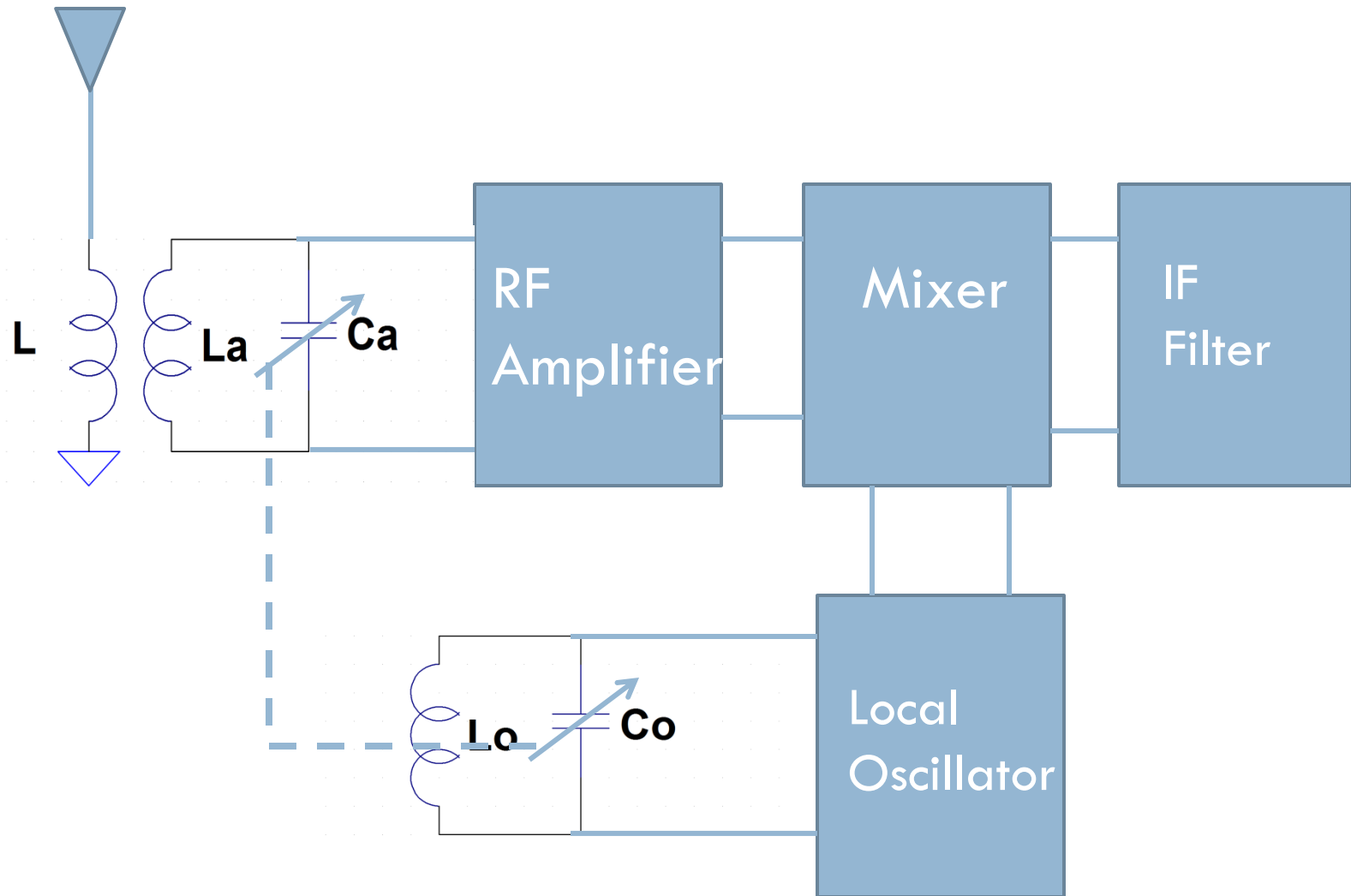

Frequency relationships

- f_a : Resonant frequency of the antenna tank circuit
Set to the carrier frequency of the desired station
- f_o : Resonant frequency of the oscillator tank circuit
- f_{if} : Intermediate frequency = $f_o - f_a$
Remains constant regardless of the station being tuned
455.5 KHz in AM : 10 KHz BW
10.7 Mhz in FM : 200 KHz BW

Advantages

- Q requirement goes down

For AM : $455.5/10 = 45.55$

For FM : $10.7/0.2 = 53.5$

- Most gain is designed at IF amplifier

Only two section gang required

Neutralization is easily achieved

Choice of intermediate frequency

- It should be outside the band of interest
- For AM radio the band is from 500 kHz to 30 MHz
Including Medium Wave and Short wave
- Above 30 MHz the Q requirement is too high
- So it is kept below 500 KHz
- Should be as large as possible to keep image interference low

Choice of local oscillator frequency

- f_0 can be chosen to be higher than f_c or lower than f_c
- Chosen higher than f_c
- Why ?
- Consider Medium wave band
500 KHz to 1500 kHz
- If chosen higher
$$f_{0\min} = 500 + 455.5 = 955.5 \text{ kHz}$$
$$f_{0\max} = 1500 + 455.5 = 1955.5 \text{ kHz}$$
- Ratio of $f_{0\max}$ to $f_{0\min}$ is approx. 2

Smaller local oscillator frequency

- $f_{0\min} = 500 - 455.5 = 44.5 \text{ kHz}$
- $f_{0\max} = 1500 - 455.5 = 1044.5 \text{ kHz}$
- So the ratio of $f_{0\max}$ to $f_{0\min}$ is greater than 20.

Tracking error

- Ideally we want $f_o - f_a = f_{if}$ at all settings of f_a
- Mechanical gang with identical gang sections
True only at one frequency (Center frequency) of the band
- At other settings there is tracking error
- Desired station is received away from f_a
- Specially shaped gang with non identical sections required
- With digital control and electronic tuning

Tracking error can
be eliminated

$$f_o - f_a = f_{if} \pm \Delta f$$

Δf is called tracking error

$$f_{if} = (f_o - f_a) \mp \Delta f$$

$$f_o - (f_a \pm \Delta f)$$

Question

- (a) In a radio receiver using identical gang sections find antenna tank coil inductance at gang setting of $C = 175 \text{ pF}$ and $f_a = 1000 \text{ kHz}$. Next calculate oscillator coil inductance assuming there is no tracking error.
- (b) Using above coils if the gang capacitor is set to 150 pF find the tracking error

Answers

□ $L_a = 144.7445 \mu\text{H}$

□ $L_o = 68.32471 \mu\text{H}$

□ $A_t C = 150 \text{ pF}$

$$f_a = 1.080124 \text{ MHz}$$

$$f_o = 1.57212 \text{ MHz}$$

$$f_o - f_a = 0.491996 \text{ MHz}$$

$$\text{Tracking error} = 0.491996 - 0.45555 = 0.036446 \text{ MHz}$$

Image frequency in a radio receiver

- The antenna tank circuit has low Q

Hence it allows many signals to go to the input of converter

But only those signals which generate f_{if} will go to the output

$$f_o - f_c = f_{if} \quad : \quad f_o = f_c + f_{if}$$

Now consider a frequency $f_i = f_c + 2f_{if}$

So output frequency is $f_i - f_o = f_c + 2f_{if} - f_c - f_{if} = f_{if}$

- So f_i causes interference and is called image frequency

Reducing the effect of image

- Tuned circuit ahead of mixer
- Larger the IF frequency easier it is to reject the image frequency

Problem

- A varactor tuned antenna tank circuit has a resonant frequency of 1400 KHz
- $L = 145$ microhenries
- The varactor characteristic is linear and two points on this are given below


V (Volts)	C(pF)
3.5	192
6	61

- Find C and V

Answers

- $C = 89 \text{ pF}$
- $V = 5.48 \text{ volts}$

Automatic gain control(AGC)

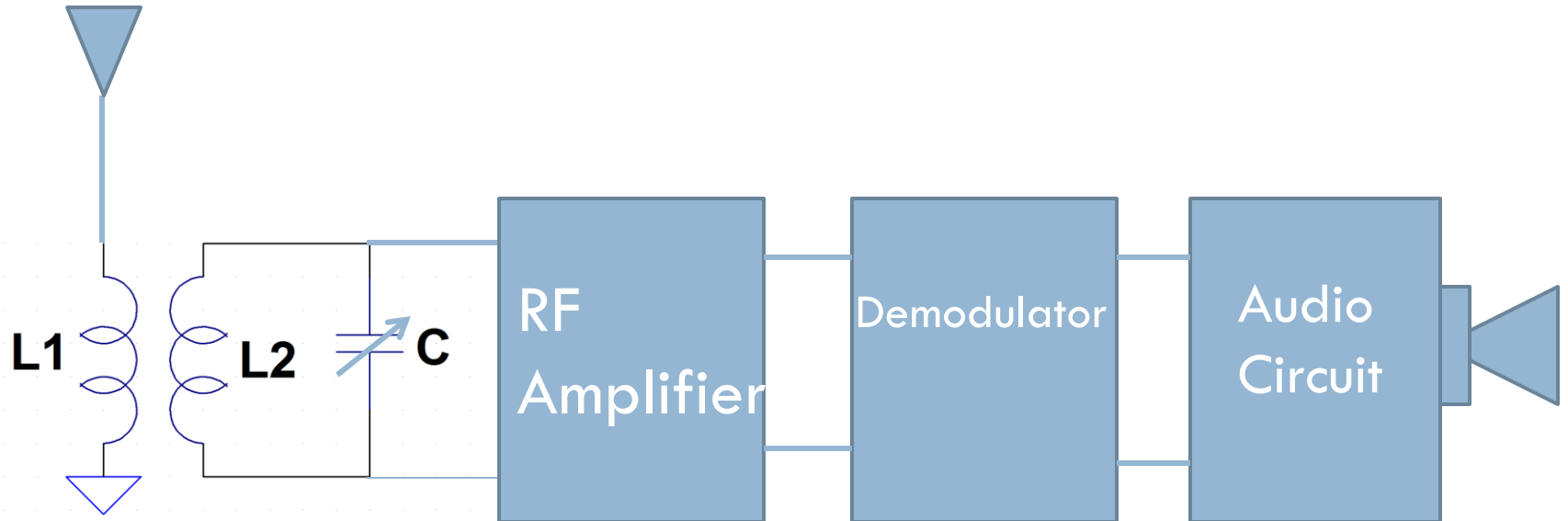

Stages in a Software defined radio

- Front End

 - Low noise amplifier

 - Down converter

 - A/D converter

- Processor

- D/A converter

LNA

- Output of Receiving antenna goes to the input of a low noise amplifier
- In a multistage cascade the first stage noise is dominant so it has to be carefully designed

For example consider 4 stages of amplification

The noise added by the first transistor is amplified by 3 stages

Noise added by the second stage is amplified only by 2 stages

Low noise stage



- Low noise transistor is chosen
- Operated at comparatively small bias currents