

QUIZ 1



Question 1

- A series resonant circuit consisting of R-L-C elements is driven by a voltage source given by $v = V \sin \omega t$. Do the following
- (a) Write down the expression for resonant frequency (Hz) in terms of L and C
- (b) Write down the expression for the instantaneous current $i(t)$ at resonance
- (c) Obtain the complex expression for current at a frequency which is $1.5 \omega_0$ in terms of current at resonance and Q

Solution to Question 1

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

At resonance


$$i(t) = \frac{V}{R} \sin \omega t$$

At $\omega = 1.5\omega_0$

$$\begin{aligned} I &= \frac{V}{R \left(1 + jQ \left[\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right] \right)} = \frac{I_0}{\left(1 + jQ \left[1.5 - \frac{1}{1.5} \right] \right)} \\ &= \frac{I_0}{(1 + jQ[0.833])} \end{aligned}$$

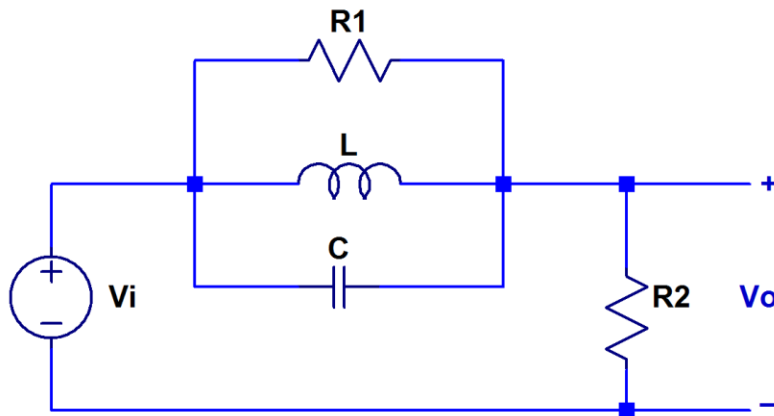Question 2

- For the circuit shown below find the voltage gain (With brief explanation) at
- (1) Zero frequency
- (2) Infinite frequency
- (3) Resonant frequency
- (4) Discuss the nature of filter if $R1 \gg R2$
-



Solution to Question 2

- (1) Gain = 1 since inductor is short circuit for DC
- (2) Gain = 1 since capacitor is short circuit at infinite frequency
- (3) $Gain = \frac{R_2}{R_1 + R_2}$
Since L-C circuit is open at resonance
- (4) Works like a band reject filter since gain is small at resonant frequency

Question 3

- Consider a 5 stage synchronously tuned amplifier and derive the expression for the overall bandwidth in terms of bandwidth of individual stages starting with the complex gain for an individual stage as a function of frequency

Solution to Question 3

$$|A| = \frac{A_0^5}{\left(\sqrt{1+x^2}\right)^5}$$

$$\text{At } x = x_c$$

$$|A| = \frac{A_0^5}{\sqrt{2}} : \left(\sqrt{1+x_c^2}\right)^5 = \sqrt{2}$$

$$\left(\sqrt{1+x_c^2}\right) = \left(\sqrt{2}\right)^{1/5}$$


$$1+x_c^2 = 2^{1/5}$$

$$x_c = \sqrt{2^{1/5} - 1} = 0.386$$

Question 4

- Consider the oscillator circuit shown below.
-
- Suppose $R4 = 2 R3$
- (a) Find the ratio of $R2$ and $R1$ to satisfy Barkhausen criterion
- (b) Let the output of the Op-Amp be $V1$.
- Now consider a nonlinearity in either $R4$ or $R3$ and because of that the ratio $R4/R3$ decreases with $V1$ linearly . One point on this line is $R4/R3 = 3$ and $V1 = 1$ volts .The other point on this line is given as $V1 = 4$ and $R4/R3 = 1$. Initially the ratio of $R4/R3$ is kept greater than 2 so the oscillations grow.
- Find the stabilized amplitude ($V1$).

Question 4 continued

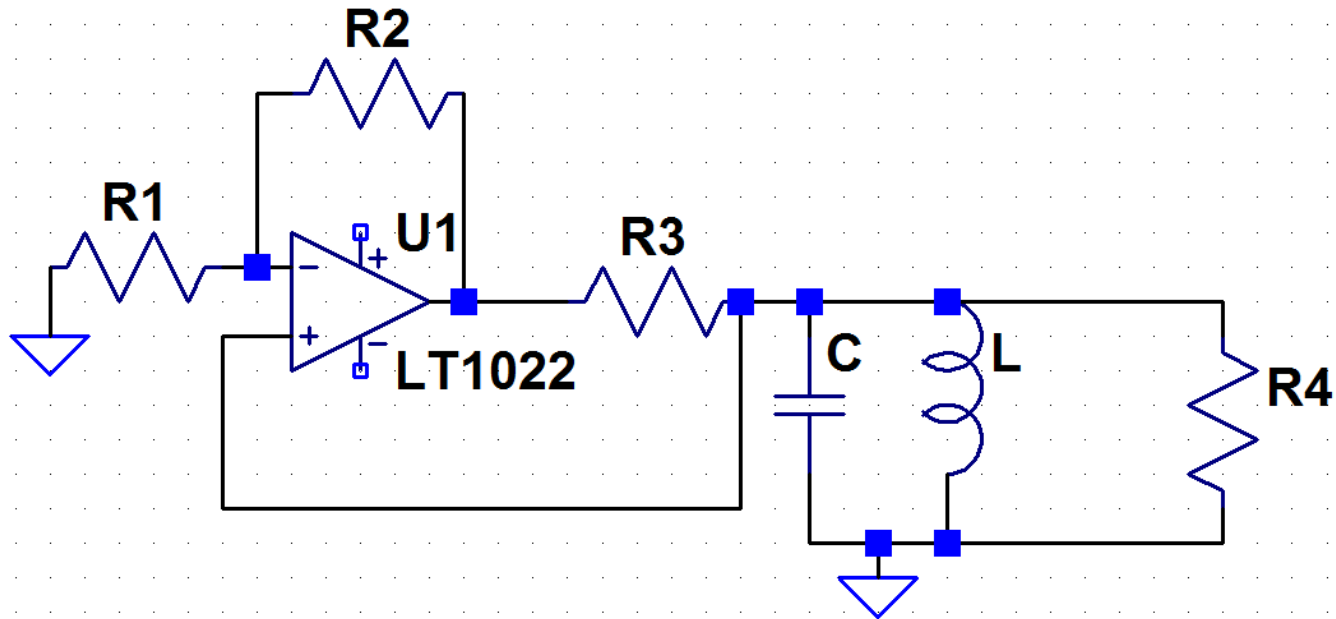


Solution to Question 4

$$\beta = \frac{R_4}{R_3 + R_4} = \frac{2R_3}{R_3 + 2R_3} = \frac{2}{3}$$

$$A_{\min} = \frac{1}{\beta} = \frac{3}{2}$$

$$1 + \frac{R_2}{R_1} = 1.5 \therefore \frac{R_2}{R_1} = 0.5$$

Solution to 4 continued

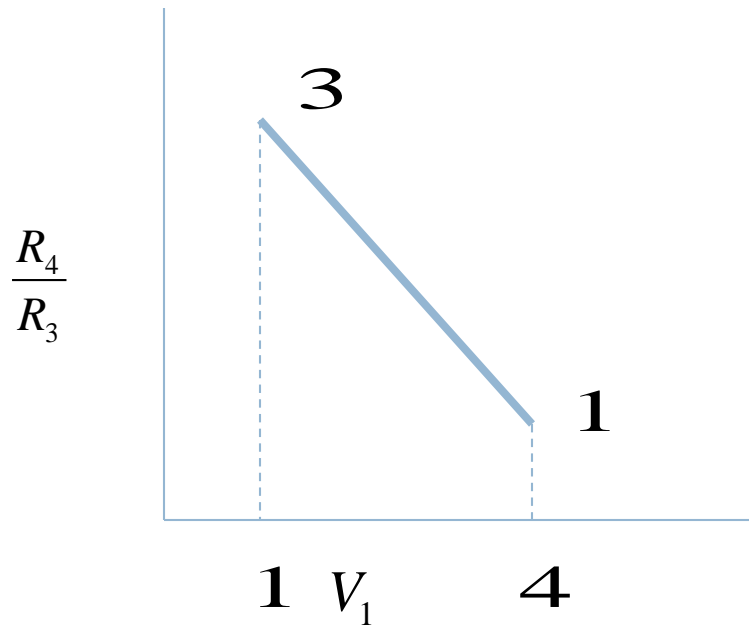

$$\frac{R_4}{R_3} = -\frac{2}{3}v_1 + C$$

$$3 = -\frac{2}{3} + C : C = \frac{11}{3}$$

$$\frac{R_4}{R_3} = -\frac{2}{3}v_1 + \frac{11}{3}$$

At $\frac{R_4}{R_3} = 2$ the amplitude stabilizes

$$2 = -\frac{2}{3}v_1 + \frac{11}{3}$$

$$v_1 = 2.5$$

Question 5

- A 100 KHz sinusoidal signal is connected to the cascade of following blocks
- (1) Two frequency doublers in cascade
- (2) An up converter with local oscillator frequency of 150 KHz
- (3) A frequency tripler
- Find the frequency of the output signal

Solution to Question 5

Output of first block

$$f_1 = 100 \times 4 = 400 \text{ KHz}$$

Output of second block

$$f_2 = 400 + 150 = 550 \text{ KHz}$$

Output of third block

$$f_3 = 550 \times 3 = 1650 \text{ KHz}$$

Question 6

Consider the antenna tank circuit and the oscillator circuit in a radio receiver. Now instead of using a gang capacitor suppose you use discrete capacitors to tune to three stations . You will require a mechanical multipole multiway switch . How many poles and how many ways you need? Draw the circuit. What will be the advantage of this arrangement over using identical gang capacitor ? What will be the disadvantage ?

Solution to Question 6

