

# OSCILLATORS

## Lecture 5


# Oscillator

- Oscillator is a circuit that produces a time varying waveform using the d.c. input
- Sinusoidal oscillator

A

*Condition for oscillation*

$$A\beta = 1 \angle 0$$

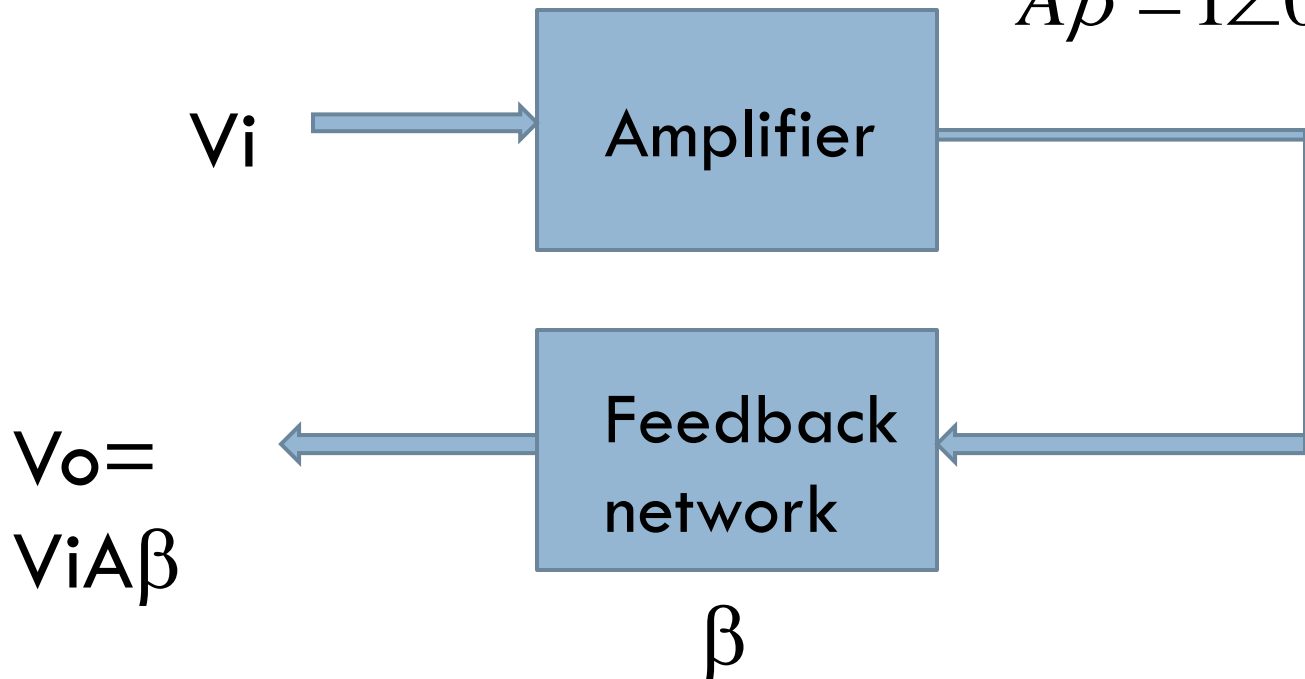


# Loop gain

- $A\beta$  is called a loop gain.


It is kept slightly higher than 1

So initially the oscillations grow

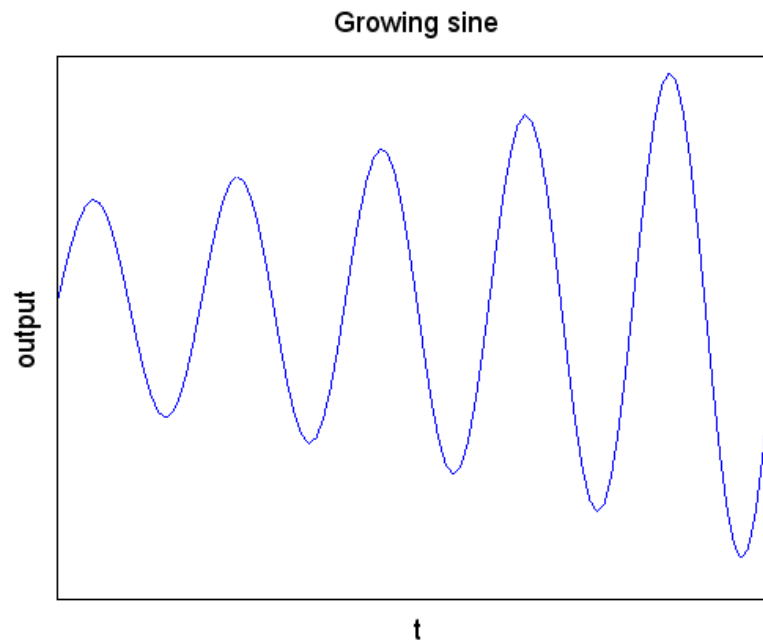

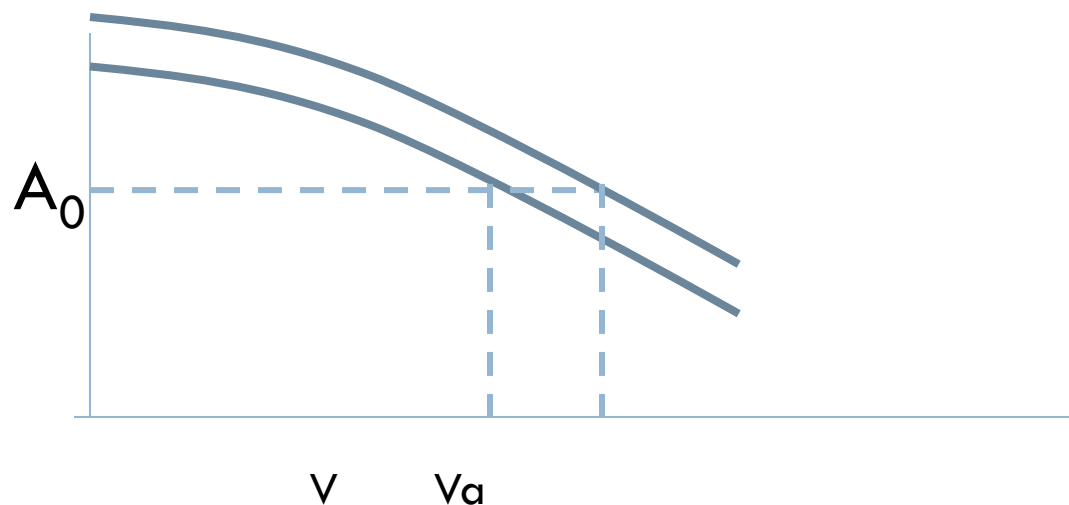
# Amplitude stabilization

- Due to non-linearity in the circuit  $A$  falls as amplitude increases
- The amplitude stabilizes when  $A\beta$  becomes unity
- The frequency of oscillations is the frequency at which the phase shift becomes zero.
- $A_0\beta = 1$



# L-C oscillator

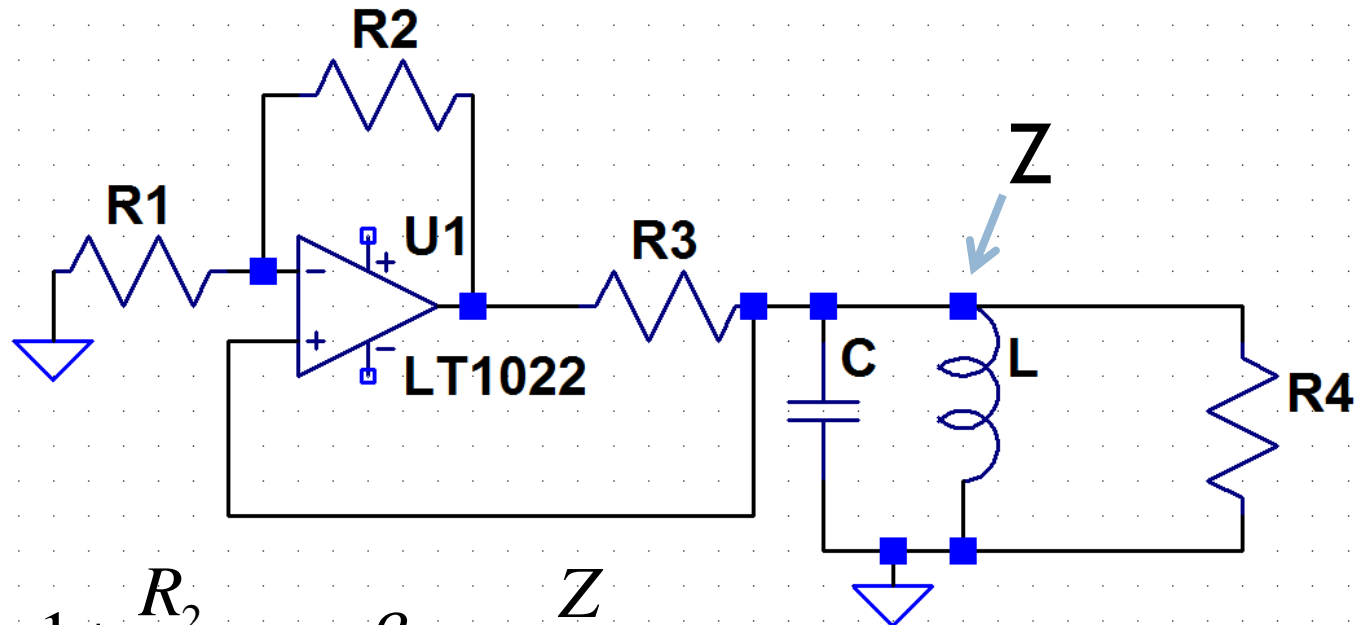

$$A = 1 + \frac{R_2}{R_1} \quad \beta = \frac{Z}{R_3 + Z}$$

Note that  $A$  has an angle of zero and  $\beta$  has zero angle at resonance so the Barkhausen criterion is satisfied and the circuit oscillates at resonant frequency

# Minimum gain requirement


$A_{\min} \beta = 1 : \text{At resonance}$

$$A_{\min} = \frac{1}{\beta} = \frac{R_3 + R_4}{R_4}$$

*Frequency of oscillations*

$$f_0 = \frac{1}{2\pi\sqrt{LC}}$$

# Problem

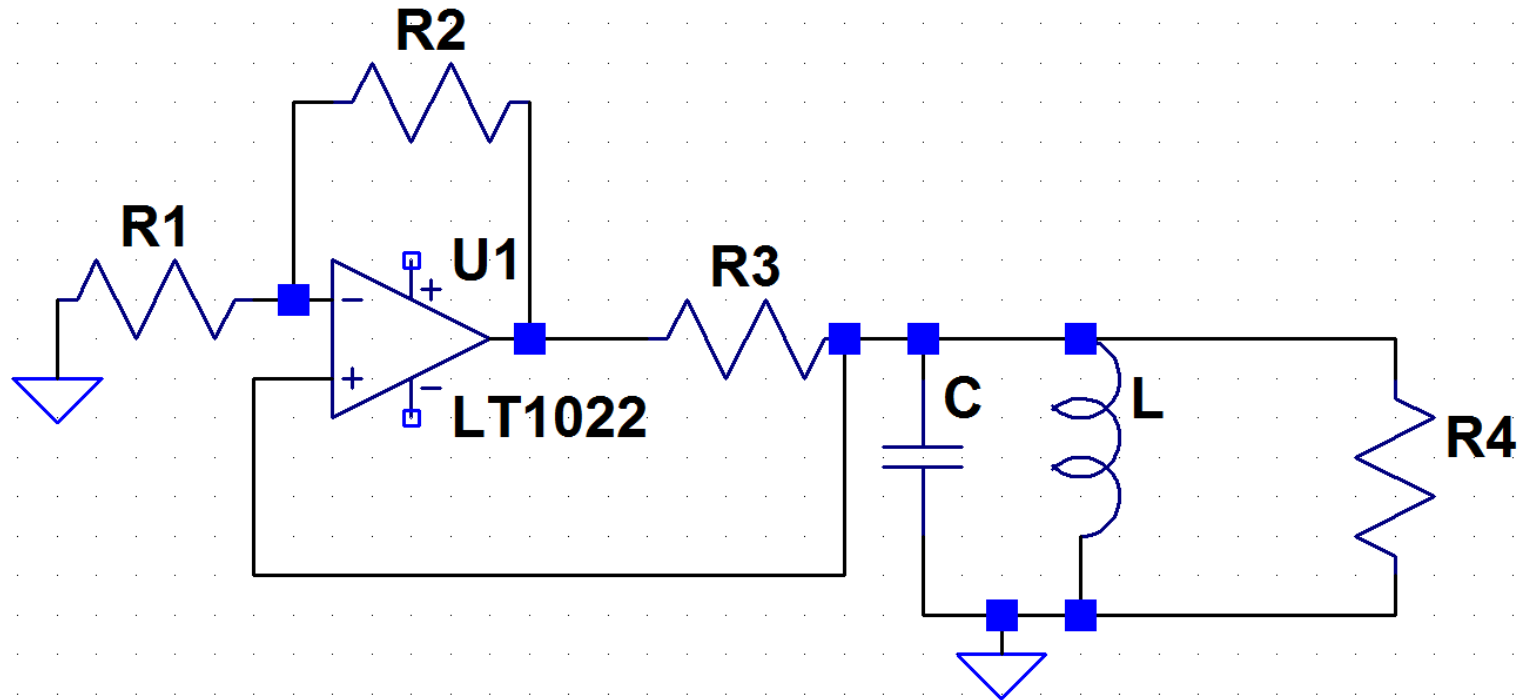

$$R3 = R4$$

Find the ratio of R2 to R1 to satisfy Barkhausen criterion

$L = 100 \mu\text{H}$  and  $C = 100 \text{ pF}$


Find the frequency of oscillations

# Answers





# Amplitude limiting in oscillators

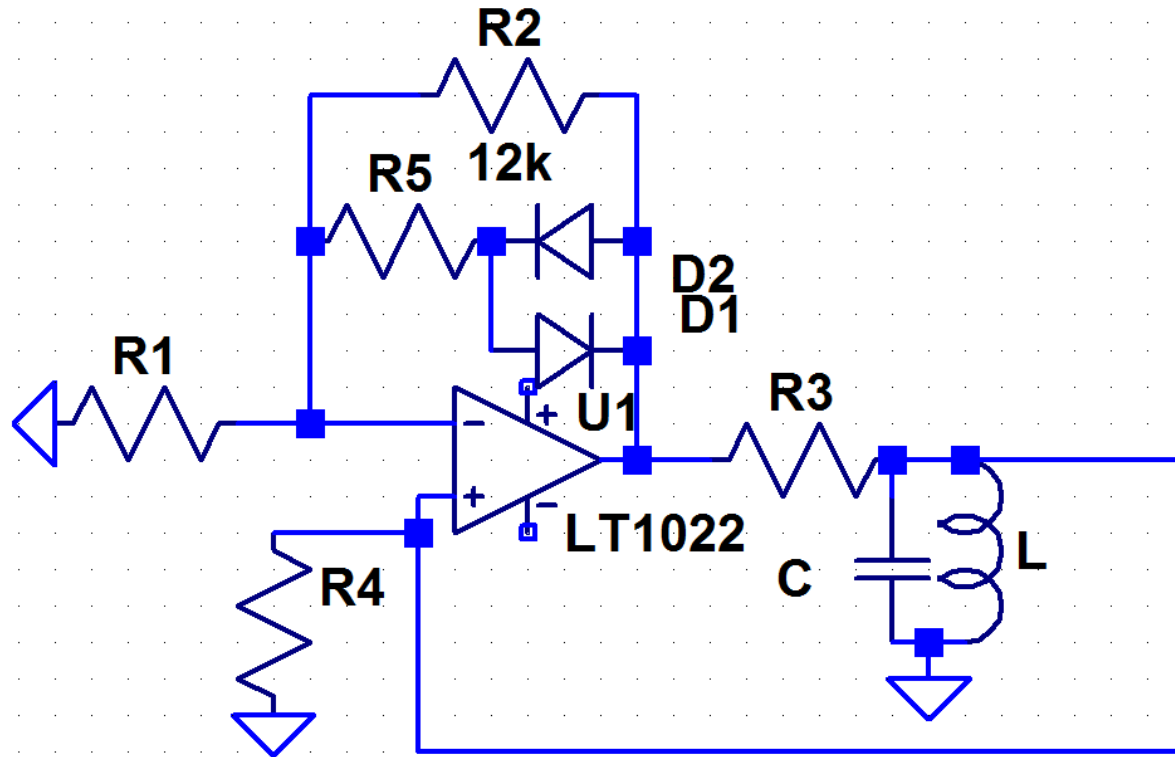


Design the above circuit for oscillating at 1.59 MHz. Diodes used are for limiting amplitude. Chose A slightly greater than  $A_{min}$ . And chose R5 much larger than R2 to keep distortion low.

# Problem

---


- Build an oscillator circuit using a series resonant circuit

# Oscillator with amplitude limiting

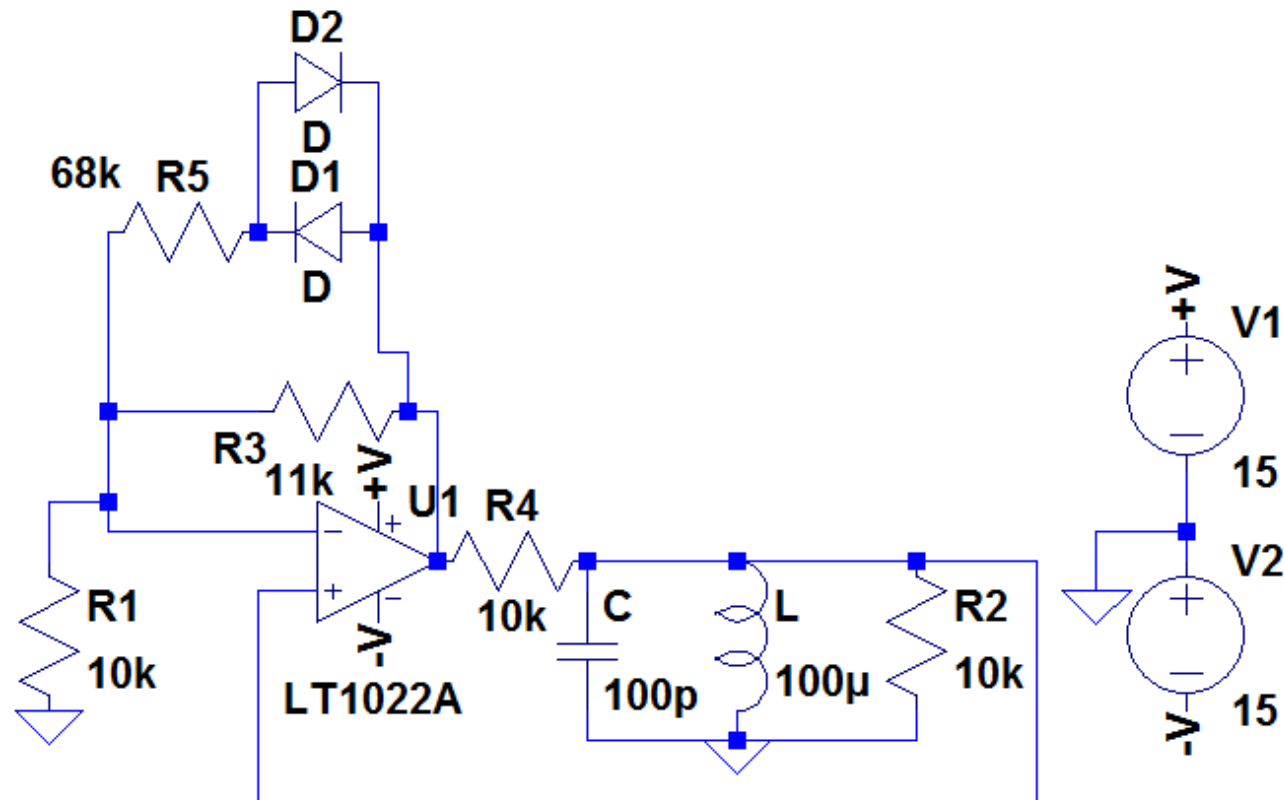


.tran 1000u startup

# Output waveform

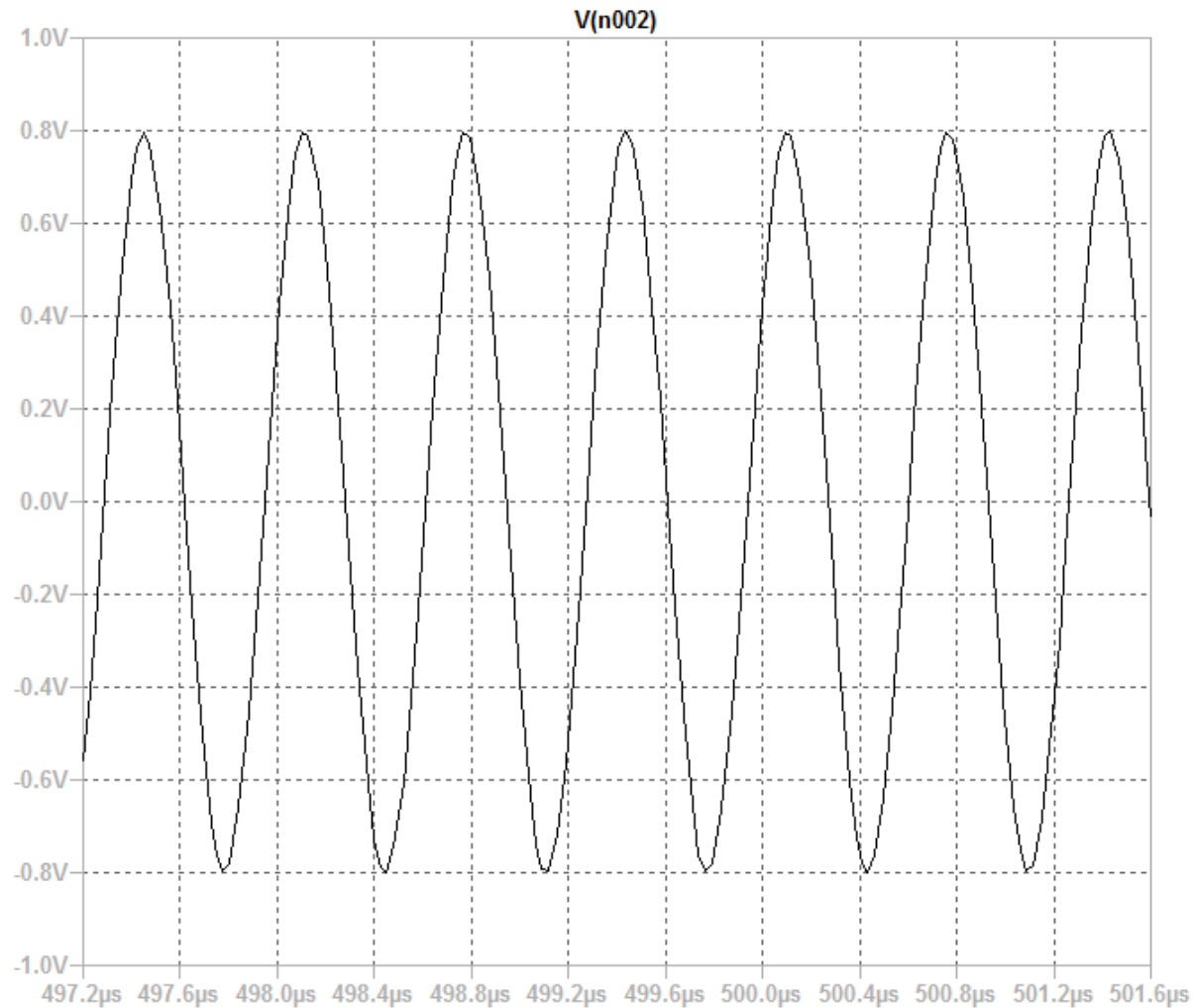

# An RF oscillator circuit

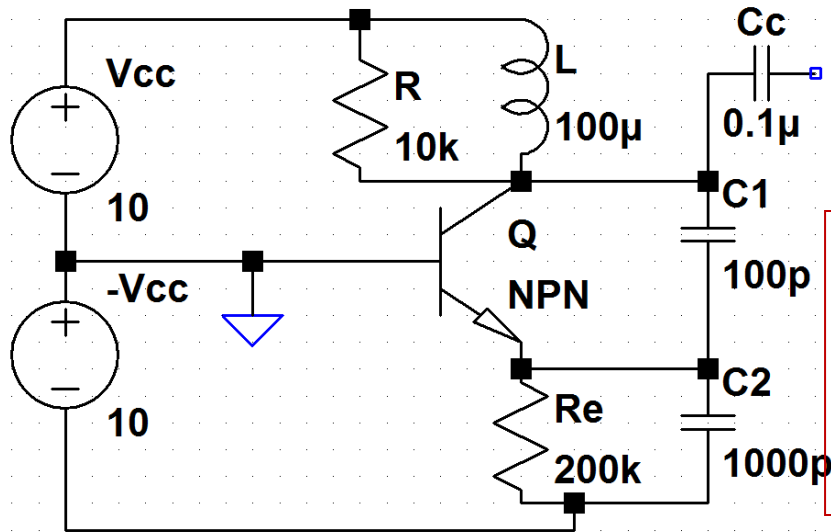

*Frequency of oscillations is*

$$f_0 = \frac{1}{\sqrt{LC}} \quad \text{where } C = \frac{C_1 C_2}{C_1 + C_2}$$

Common base amplifier

C1 and C2 form the feedback circuit

Amplifier gain can be controlled by R